

McGILL UNIVERSITY

ECSE 335

MICROELECTRONIC LABS

2.1 - Differential Amplifier (Prelab)

Authors (Group 14):

John Wu

Ian Smith

Bilal Yousuf

Student Number:

260612056

260634831

260680182

October 29, 2018

2.1 Preparation

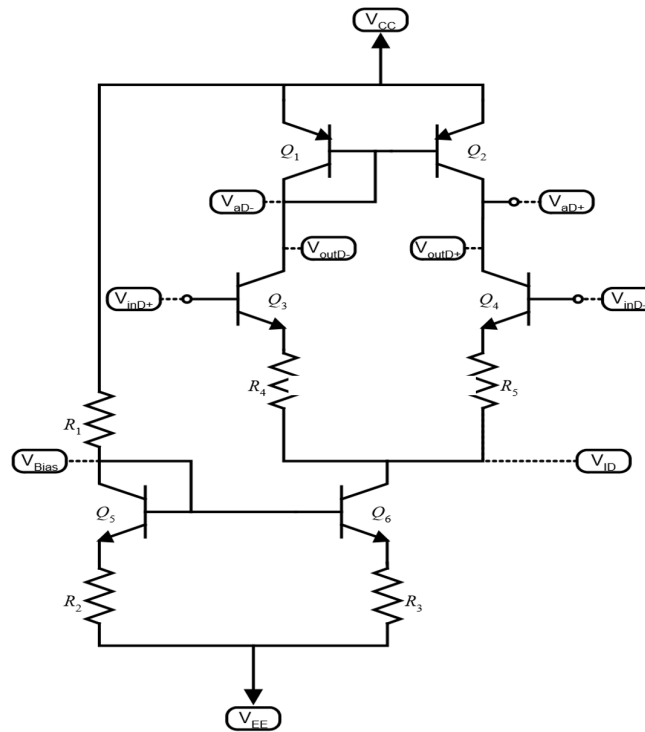


Figure 1: Differential amplifier with active load

2.1.2 Considering this circuit will be used as an output stage in an operational amplifier, what are the main characteristics that it must have?

Since the circuit will be used as an output stage in an operational amplifier, it must have the following characteristics in its most ideal form.

- Infinite open-loop gain.
- Infinite bandwidth due to ideal gain.
- Infinite or zero common mode rejection ratio (CMRR).
- Infinite input impedance.
- Zero output impedance.

In general, these ideal characteristics will not be the actual case, but it will aim to be as close to these idealistic values as possible in order to deliver large currents to a small load - the goal of an op-amp.

2.1.3 What is the purpose of R_2 and R_3 ?

The resistors, R_2 and R_3 , are source degeneration resistances used for creating a higher output impedance and a lower equivalent transconductance. These resistors are used to give a high resistance to the current mirror formed by Q_5 and Q_6 . The high output resistance will reduce the common mode gain and improve the CMRR. The resistors prevent thermal runaway in transistors Q_5 and Q_6 thereby providing thermal stability.

2.1.4 Using $V_{EE} = -5V$ and $V_{CC} = 5V$, design the current source of the differential pair so that it sinks a current of $0.25mA$. Determine the required value of R .

When $R_2 = R_3 = 2k\Omega$ and Q_5 and Q_6 make perfect current mirrors:

$$I = \frac{V_{EE} - V_{BE} - V_{CE}}{R_2 + R_1}$$

$$\frac{9.3V}{2k\Omega + R_1} = 0.25mA$$

$$R_1 = 35.2k\Omega$$

2.1 - Differential Amplifier (Prelab)

2.1.5 Considering the current source only, plot the source's output current versus the output voltage and comment on the results.

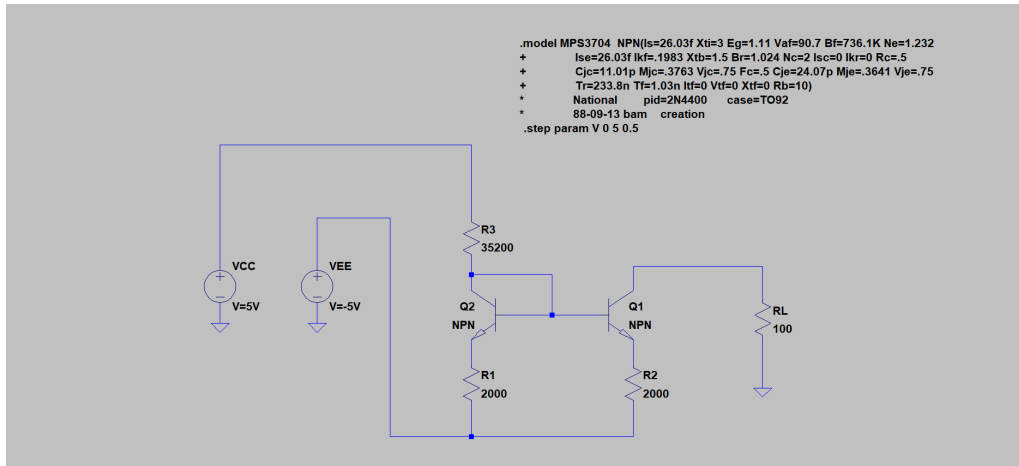


Figure 2: Circuit used for analyzing output.

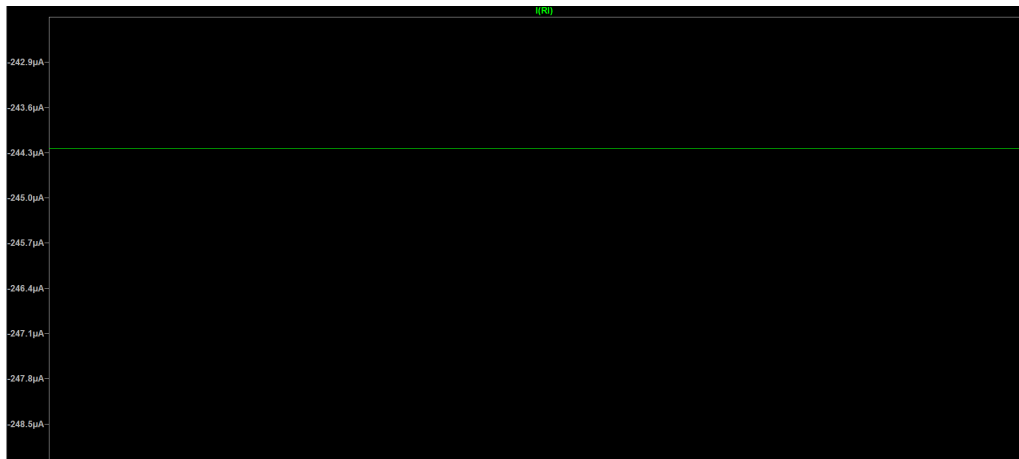


Figure 3: Output current versus output voltage graph.

It can be observed that the output current reaches the expected constant value of approximately 0.25mA regardless of the output voltage.

2.1.6 Design the circuit of Figure 2.1 in order to obtain a gain of $250V/V \pm 10\%$. Determine the values of R_4 and R_5 . Discuss. At the output, take into account the loading caused by a $10X$ oscilloscope probe.

$$r_e = \frac{V_T}{I_C/2} = \frac{2*25mV}{0.25mA} = 200\Omega$$

$$r_{o2} = \frac{V_A}{I_C/2} = \frac{2*115.7V}{0.25mA} = 925.6k\Omega$$

$$r_{o4} = \frac{V_A}{I_C/2} = \frac{2*90.7V}{0.25mA} = 725.6k\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0.125mA}{25mV} = 5mA/V$$

$$A_d = \frac{r_{o4}(1+g_m R_4)||r_{o2}||R_{OSC}}{r_e + R_4}$$

We consider $R_{OSC} = 10\text{ M}\Omega$.

R_4 is approximately $1.36k\Omega$. We'll make $R_5 = R_4 = 1.36k\Omega$

2.1.7 Plot the voltage transfer characteristics and accompany it with the corresponding time domain waveform plot. Discuss the curve and maximal output swing.

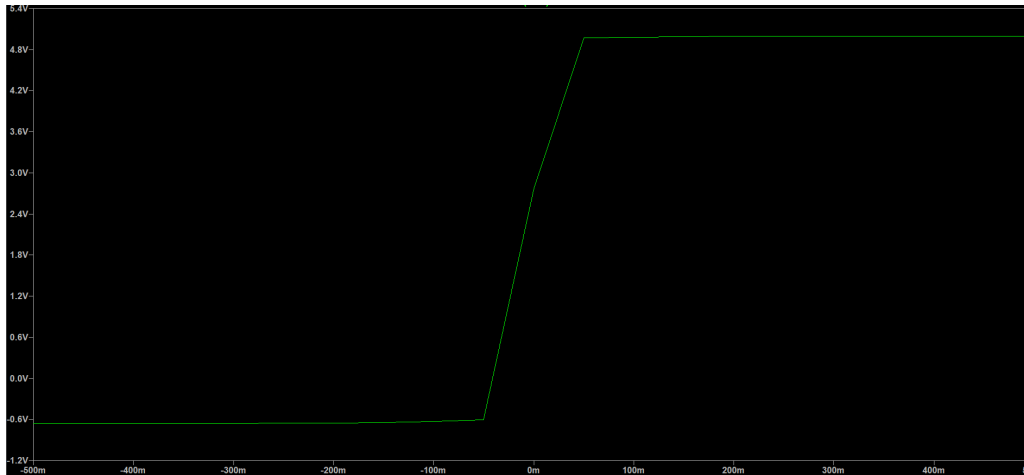


Figure 4: Voltage transfer characteristics.

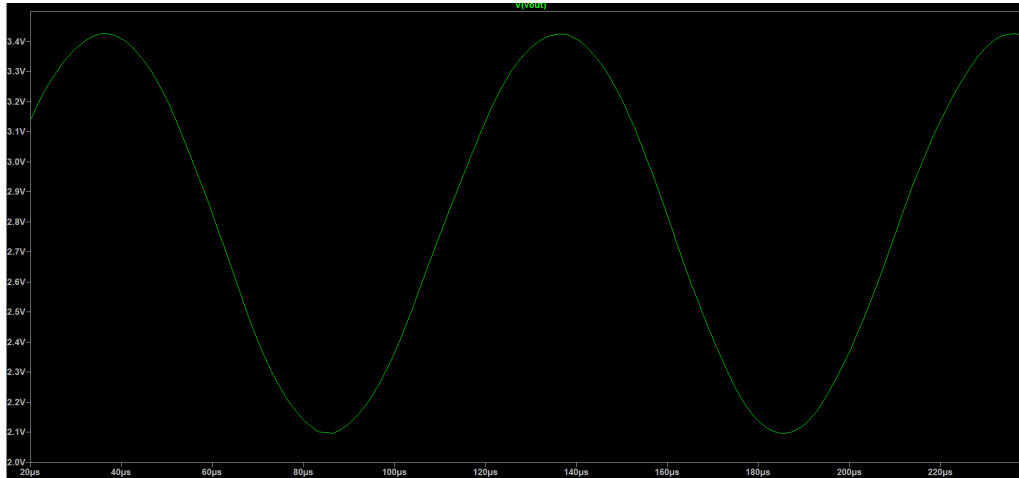


Figure 5: Time domain waveform.

We can observe that maximal output swing centers at around 2V and occurs at input signals between -50mV and 50mV.

2.1.8 Determine, if any, the input DC offset required to maximize the output swing. Document the maximum output swing. Discuss.

The max DC offset that results in the maximum output voltage swing occurs at the centre of the steepest part of the curve. As mentioned above, this offset value is around 2V.

2.1.9 Plot the differential mode frequency response and determine the 3 – dB points. Also, take into account the parasitic resistor and capacitor values of the 10X oscilloscope probe at the output. Discuss.

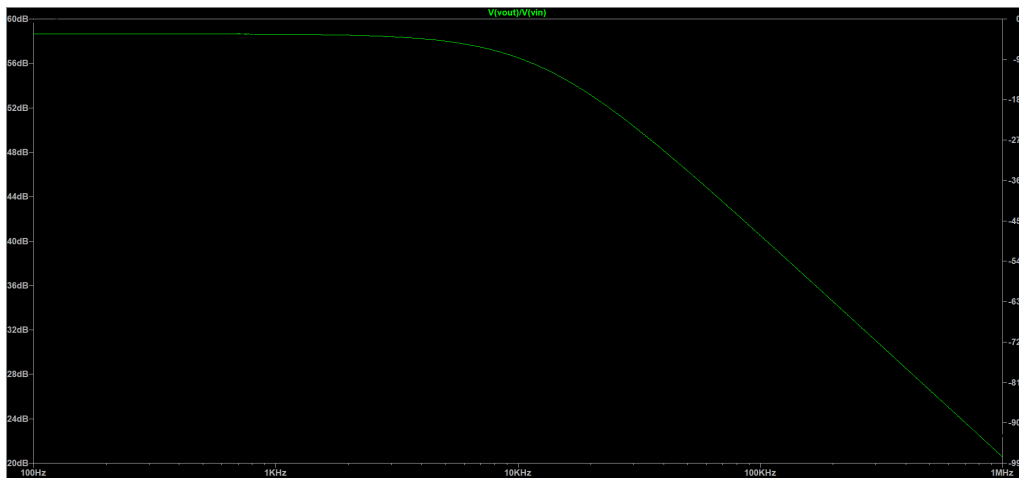


Figure 6: Differential mode frequency response.

We can observe above that the differential gain about 59 dB (891 V/V) and the 3 dB cutoff frequency is about 13 KHz.

2.1.10 Plot the common mode frequency response. Also, take into account the parasitic resistor and capacitor values of the 10X oscilloscope probe at the output. Discuss.

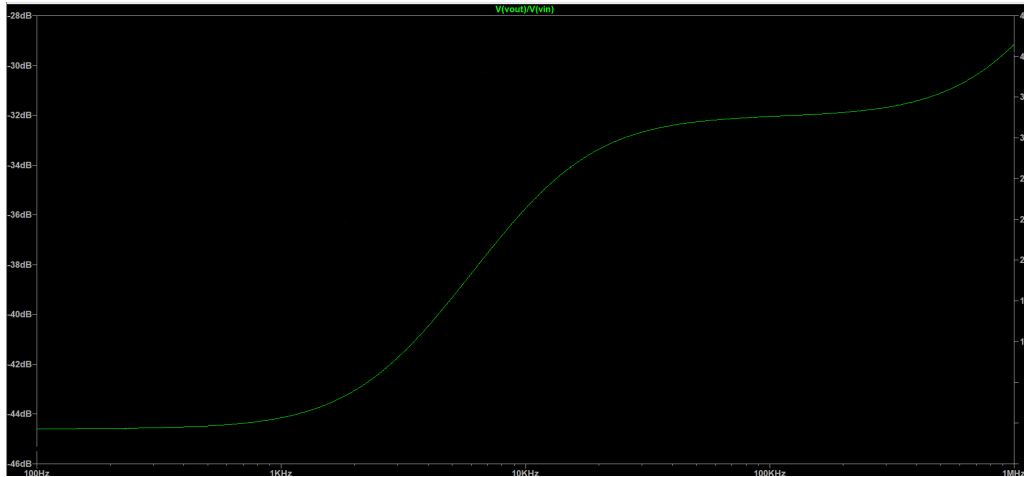


Figure 7: Common mode frequency response.

The common mode gain is about -30 dB (0.03 V/v), which is significantly lower than our differential gain, and therefore meets the requirements of the circuit.

2.1.11 Find the input and output resistances the circuit. Discuss.

$$R_{in} = 2(\beta + 1)(r_e + R_4) = 2(100 + 1)(200 + 1.36k) = 315.3k\Omega$$

$$R_{out} = r_{o2} || r_{o4}(1 + g_m R_5 || r_\pi) = 925.6k || 725.6k(1 + 0.005(1.36k || 20k)) = 795.4k\Omega$$

For R_{out} the resistance of the 10X probe was not considered in the calculation since it is large enough that we can neglect it.

2.1.12 In summary, what are the advantages and limitations of this circuit setup?

The advantages of this circuit are that it gives a high gain with a flexible voltage swing. The limitations are that there is a large output resistance with a narrow bandwidth.